

EE671: VLSI Design

Assignment 5

Sai Saketika Chekuri
190070054

November 1, 2022

The following delays are used for the logic gates required.

Function	Delay (in ps)
AND	44
$A + B.C$	58
XOR	68
$A.B + C.(A + B)$	68

Design

- Initially, the maximum number of partial product bits in any column is 9.
- We need 4 stages of reduction ($9 \rightarrow 6 \rightarrow 4 \rightarrow 3 \rightarrow 2$)
- For each stage of reduction, as per the Dadda algorithm, we choose the least number of smallest adders required so that the capacity of the next stage is not exceeded.
- From the dot diagram below, we see that 48 ($8 + 16 + 11 + 13$) Full Adders and 8 ($4 + 2 + 1 + 1$) Half Adders are needed.
- Once we reduce it to 2 vectors, we use a 16-bit logarithmic Brent Kung adder to obtain the final MAC sum and carry results

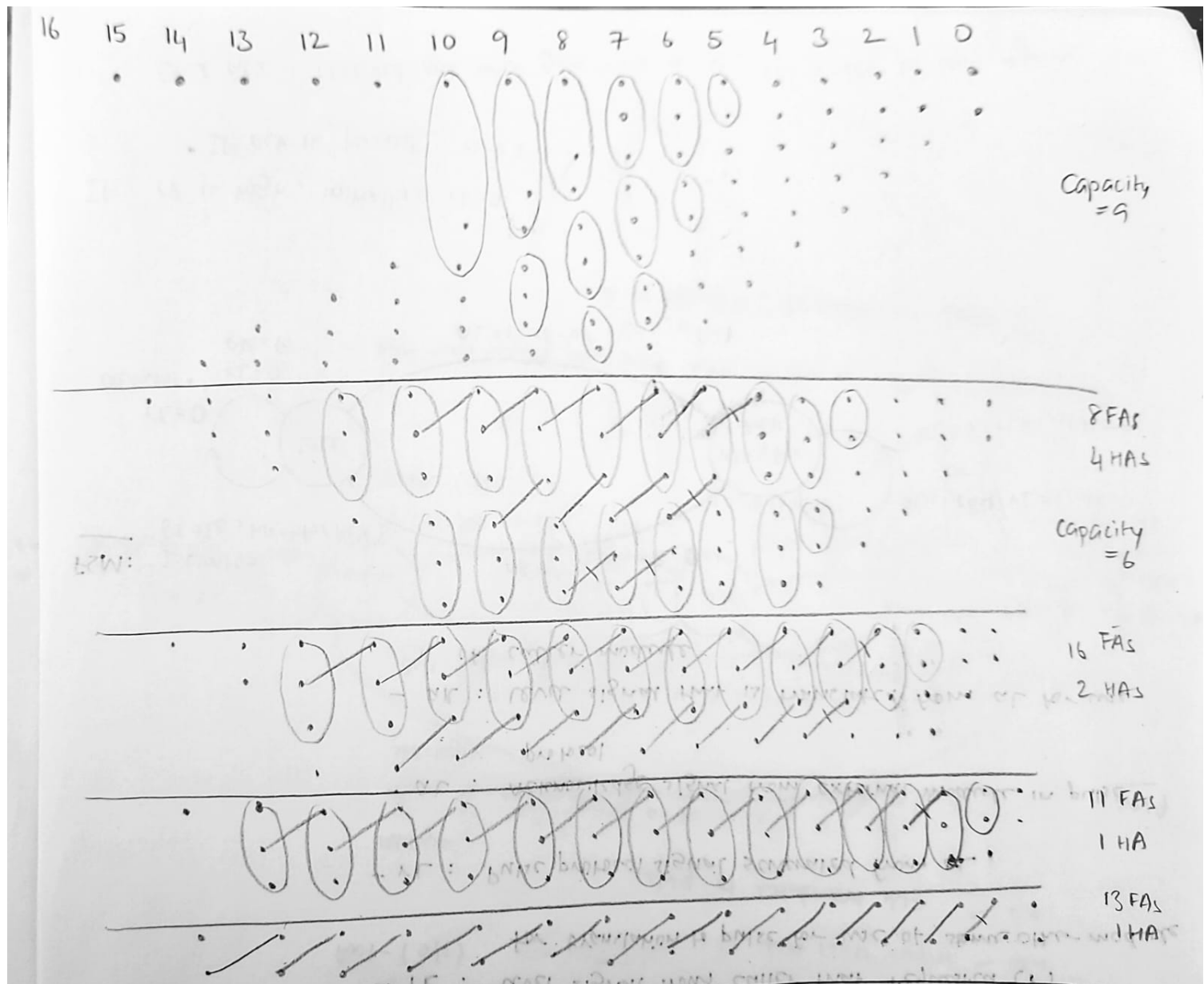


Figure 1: Dot Diagram for Dadda MAC

Testbench

The trace file has two vectors, one with appended inputs (A and B are 8-bit inputs to be multiplied, and C is a 16-bit number to be added to this product) and the other with carry-out and sum appended.

- Vector 1: A B C (32 bits)
- Vector 2: Cout Sum (17 bits)

This appending is done by DUT, which instantiates a MAC component.

The testbench py file generates 'TRACEFILE.txt', which contains 10 randomized test-cases (including corners cases where all have minimum, maximum and complementary values).

Results

- Delay in RTL simulation $\approx 800ps$
- Delay in Gate Level simulation $\approx 23ns$

 


Figure 2: RTL Simulation

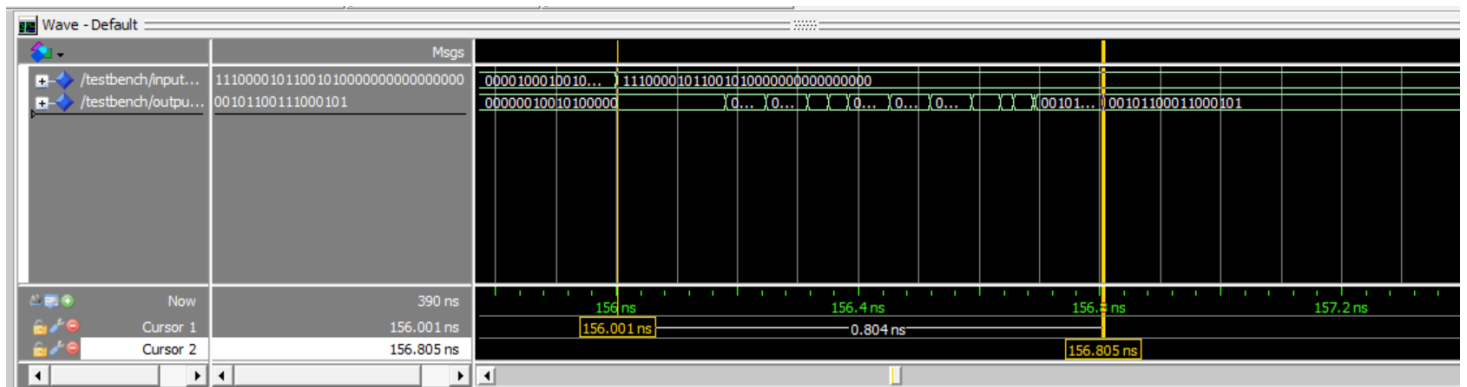


Figure 3: Delay in RTL Simulation

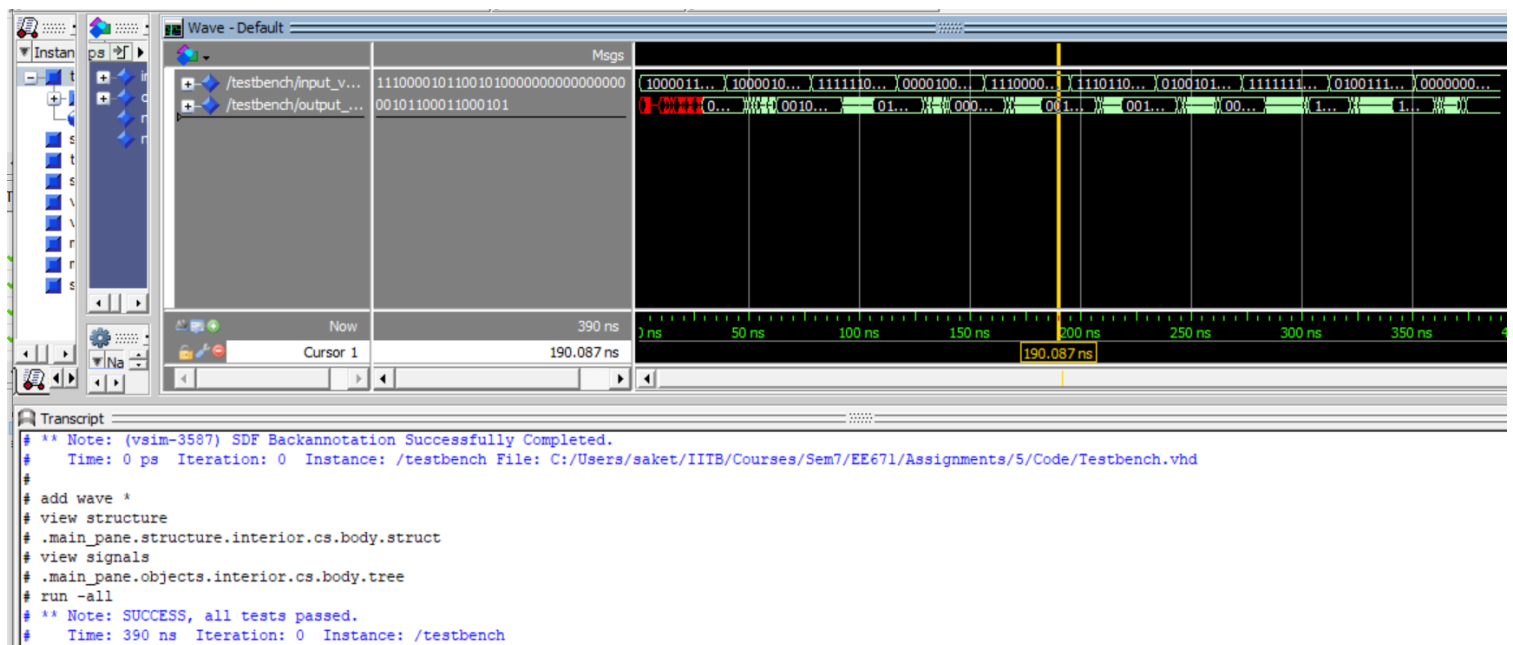


Figure 4: Gate Level Simulation

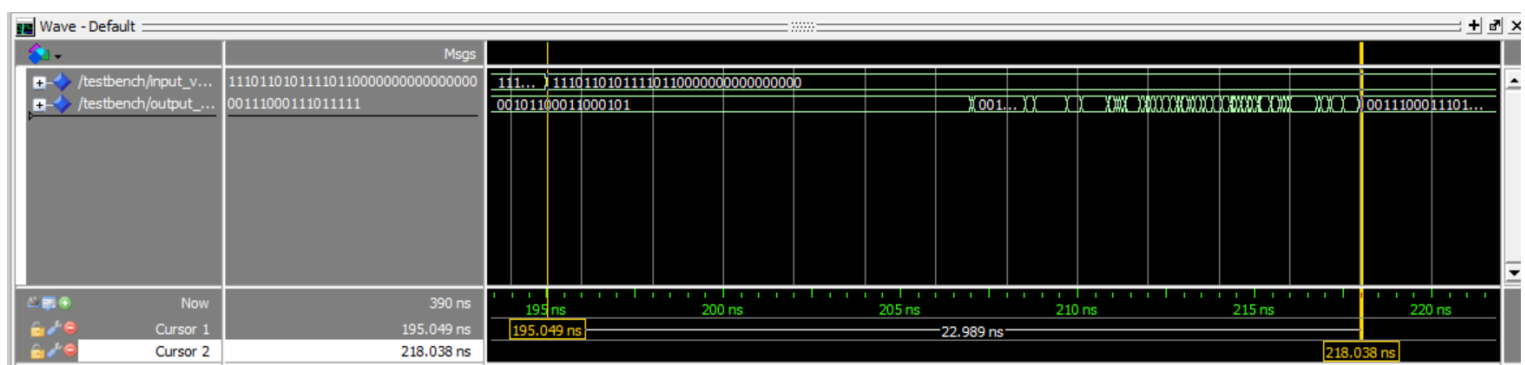


Figure 5: Delay in Gate Level Simulation